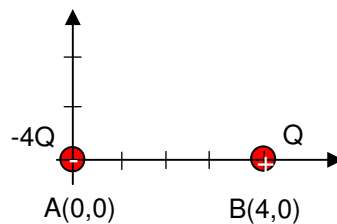


1. (2,5 points) Given the point charges  $-4Q$  and  $Q$  on picture, placed at points  $A(0,0)$  m and  $B(4,0)$  m:
- (1) Find a point  $P$  of  $X$  axis where the electric fields due to both charges are cancelled (total electric field zero).
  - (1) Find a point  $P'$  of  $X$  axis where the electric potentials due to both charges are cancelled (total electric potential zero).
  - (0,5) Compute the work done by the forces of the electric field to carry a  $-Q$  point charge from above point  $P$  to point  $P'$ .

1. (2,5 puntos) Dadas las cargas puntuales  $-4Q$  y  $Q$  de la figura, situadas en los puntos  $A(0,0)$  m y  $B(4,0)$  m:
- (1) Encuentra un punto  $P$  del eje  $X$  donde el campo eléctrico total sea cero.
  - (1) Encuentra un punto  $P'$  del eje  $X$  donde el potencial eléctrico total sea cero.
  - (0,5) Calcula el trabajo hecho por las fuerzas del campo debido a ambas cargas para llevar una carga  $-Q$  desde el punto  $P$  hasta el punto  $P'$ .



- a) Electric field can only be zero at points placed on right of point  $B$ . On left to  $A$ , electric field due to  $-4Q$  is always stronger than electric field due to  $Q$ , and between  $A$  and  $B$ , both electric fields are reinforced, never cancelled. If the coordinates of such point are  $(x,0)$ , being  $x > 4$ , then must be verified that

$$k \frac{4Q}{x^2} = k \frac{Q}{(x-4)^2} \Rightarrow x = 8 \text{ m} \quad \text{Therefore} \quad P(8,0) \text{ m}$$

- b) The electric potential can only be zero at points on right of  $B$  or between  $A$  and  $B$  (electric potential is a scalar). If we consider the point  $P'$  on right of  $B$ , with coordinates  $(x,0)$ , being  $x > 4$ , must be verified that

$$k \frac{4Q}{x} = k \frac{Q}{(x-4)} \Rightarrow x = \frac{16}{3} \text{ m} \quad \text{Therefore} \quad P'(\frac{16}{3}, 0) \text{ m}$$

There is a second correct solution by taking  $P'$  between  $A$  and  $B$ . If  $(x,0)$  are the coordinates of  $P'$

$$k \frac{4Q}{x} = k \frac{Q}{(4-x)} \Rightarrow x = \frac{16}{5} \text{ m} \quad \text{Therefore} \quad P'(\frac{16}{5}, 0) \text{ m}$$

Anyone of both solutions is correct.

- c) Potential on point  $P(8,0)$  is  $V_P = k \frac{-4Q}{8} + k \frac{Q}{4} = -k \frac{Q}{4} V$  Then


$$W_{PP'} = -Q(V_P - V_{P'}) = -Q(-k \frac{Q}{4} - 0) = k \frac{Q^2}{4} \text{ J}$$

2. (1 point) A positive point charge  $Q$  is placed at the center of a hollow and electrically neutral and isolated sphere (radii  $R$  and  $2R$ ).

- (0,3) Say which are the charges appearing on inner and outer surface of sphere.
- (0,4) By applying Gauss's law, compute the electric field at a point  $P$  placed at a distance  $r$  from the center of sphere ( $r > 2R$ ).
- (0,3) Compute the electric potential of the sphere.

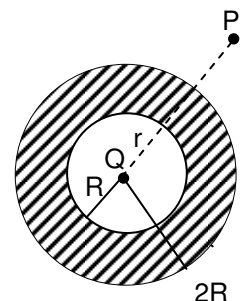2. (1 punto) Una carga puntual  $Q$  positiva está colocada en el centro de una esfera hueca y eléctricamente neutra y aislada (radios  $R$  y  $2R$ ).

- (0,3) Indica las cargas que aparecen en la superficie interior y en la superficie exterior de la esfera.
- (0,4) Aplicando el teorema de Gauss, calcula el campo eléctrico en un punto  $P$  situado a una distancia  $r$  del centro de la esfera ( $r > 2R$ ).
- (0,3) Calcula el potencial eléctrico de la esfera.



- As there is total influence between charge and sphere, a charge  $-Q$  appears on inner surface of sphere. As the sphere is isolated and it's neutral a positive charge  $Q$  must appear on outer surface.
- Due to the symmetry of problem, electric field at  $P$  will have the direction of radius and its modulus will only depend on the distance to the center of sphere. If we consider the surface of a sphere passing through  $P$  (radius  $r$ ), the electric flux through such sphere is:

$$\phi = \int_{\text{sphere}} \vec{E} \cdot d\vec{S} = \int_{\text{sphere}} E \cdot dS = E \int_{\text{sphere}} dS = E 4\pi r^2$$

According Gauss's law

$$\phi = E 4\pi r^2 = \frac{Q+Q-Q}{\epsilon_0} = \frac{Q}{\epsilon_0} \Rightarrow E = \frac{Q}{4\pi\epsilon_0 r^2}$$

c) If we consider a point placed at the outer surface of sphere and we compute its difference of potential related to the infinite is:

$$V_{2R} - V_{\infty} = \int_{2R}^{\infty} \vec{E} d\vec{r} = \int_{2R}^{\infty} \frac{Q}{4\pi\epsilon_0 r^2} dr = -\frac{Q}{4\pi\epsilon_0 r} \Big|_{2R}^{\infty} = \frac{Q}{8\pi\epsilon_0 R}$$


$$\text{As } V_{\infty}=0, \quad V_{\text{sphere}} = V_{2R} = \frac{Q}{8\pi\epsilon_0 R}$$

**3.** (2 points) Two parallel plate capacitors, initially discharged and with equal capacitance  $C$  are connected in series to a battery giving 5 V between its terminals.

- a) (0,8) Find the electric charge on each capacitor,  $Q_1$  and  $Q_2$ .  
 b) (1,2) A dielectric with dielectric permittivity  $\epsilon_r = 3$  is inserted between the plates of one of capacitors. Compute the new charges  $Q'_1$  and  $Q'_2$  and the new potential difference  $V'_1$  and  $V'_2$  on each capacitor.

**3.** (2 puntos) Dos condensadores planos, inicialmente descargados y de la misma capacidad  $C$ , están conectados en serie a una batería que da 5 V entre sus terminales

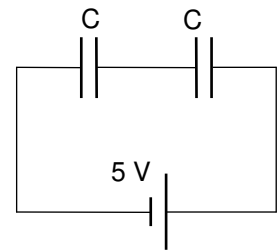- a) (0,8) Halla la carga en cada condensador,  $Q_1$  y  $Q_2$ .  
 b) (1,2) Entre las placas de uno de los condensadores se introduce un dieléctrico de permitividad relativa  $\epsilon_r = 3$ . Calcula las nuevas cargas  $Q'_1$  y  $Q'_2$  y las nuevas diferencias de potencial  $V'_1$  y  $V'_2$  en cada uno de los condensadores.



a) As both capacitors are connected in series, their charges are equal  $Q_1=Q_2$ . Then:

$$\frac{Q_1}{C} + \frac{Q_2}{C} = 5 \Rightarrow Q_1 = Q_2 = \frac{5C}{2}$$

b) When a dielectric is inserted, the capacitance of this capacitor is multiplied by  $\epsilon_r$ . Let's suppose that dielectric is inserted on capacitor 1:  $C'_1=3C$ . As both capacitors have the same charge  $Q'_1=Q'_2$ :

$$\frac{Q'_1}{3C} + \frac{Q'_2}{C} = 5 \Rightarrow Q'_1 = Q'_2 = \frac{15}{4}C$$


$$V'_1 = \frac{Q'_1}{3C} = \frac{5}{4}V \quad V'_2 = \frac{Q'_2}{C} = \frac{15}{4}V$$

**4.** (2 points) Four resistors are connected as can be seen on picture. Along  $R_4$  flows an intensity of current  $I=2$  A. Compute:

- a) (0,2) The potential difference between points A and B,  $V_A-V_B$ .  
 b) (0,2) The intensity  $I_3$  flowing along  $R_3$ .  
 c) (0,4) The potential difference between points A and C,  $V_A-V_C$ .  
 d) (0,6) The consumed power by the set of all resistors.  
 e) (0,6) If the efficiency of generator is 80%, find electromotive force and internal resistance of generator ( $\epsilon$ ,  $r$ ).

**4.** (2 puntos) Cuatro resistencias están conectadas tal y como se ve en la figura. Por  $R_4$  circula una corriente  $I=2$  A. Calcular:

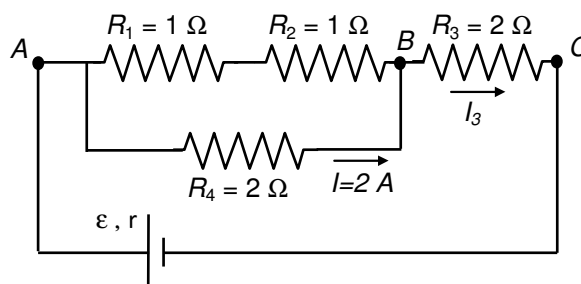- a) (0,2) La diferencia de potencial entre los puntos A y B,  $V_A-V_B$ .  
 b) (0,2) La intensidad  $I_3$  que circula por  $R_3$ .  
 c) (0,4) La diferencia de potencial entre los puntos A y C,  $V_A-V_C$ .  
 d) (0,6) La potencia total consumida por el conjunto de todas las resistencias.  
 e) (0,6) Si el rendimiento del generador es del 80%, calcula su fuerza electromotriz y su resistencia interna ( $\epsilon$ ,  $r$ ).




a) Potential difference on terminals of  $R_4$  is  $V_{R4} = V_A - V_B = I \cdot R_4 = 2 \cdot 2 = 4$  V

b) The intensity flowing along  $R_1$  and  $R_2$  is:  $I_{12} = 4/2 = 2$  A. As  $I_3 = I_{12} + I_4$  therefore  $I_3 = 2 + 2 = 4$  A.

- c) Potential difference between terminals of  $R_3$  is  $V_{R_3}=2 \cdot 4=8$  V. Therefore  $V_A-V_C=V_{R_4}+V_{R_3}=4+8=12$  V
- d) Equivalent resistance of the set of resistors is  $R_{eq}=3 \Omega$ . The consumed power:  
 $P_R = I_3^2 R_{eq} = 4^2 \cdot 3 = 48$  w
- e) The supplied power to the circuit by the generator equals the consumed power by the set of resistors and then  $P_s=48$  w. From efficiency  
 $\eta_g = \frac{P_s}{P_g} \Rightarrow 0,8 = \frac{48}{P_g} \Rightarrow P_g = \frac{48}{0,8} = 60$  w As  $P_g = \mathcal{E}I \Rightarrow 60 = \mathcal{E} \cdot 4 \Rightarrow \mathcal{E} = \frac{60}{4} = 15$  V
- Lost power on internal resistance of generator is the difference between generated and supplied power  $P_r = P_g - P_s = 60 - 48 = 12$  w And  $P_r = I^2 r \Rightarrow 12 = 4^2 r \Rightarrow r = \frac{12}{16} = \frac{3}{4} = 0,75 \Omega$

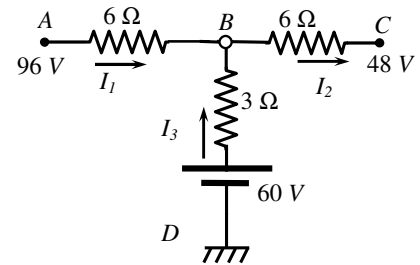5. (2,5 points) Given the circuit on picture, compute:
- a) (1,5) Intensity of current flowing along each branch of circuit with the shown senses,  $I_1$ ,  $I_2$  and  $I_3$ .
- b) (1) Difference of potential between points B and D,  $V_B-V_D$  and Thevenin's equivalent generator between points B and D, clearly showing its polarity.



2,5 points

5. (2,5 puntos) Dado el circuito de la figura, calcula:
- a) (1,5) La intensidad de corriente en cada rama con los sentidos mostrados,  $I_1$ ,  $I_2$  y  $I_3$ .
- b) (1) La diferencia de potencial entre los puntos B y D,  $V_B-V_D$ , y el generador equivalente de Thevenin entre los puntos B y D, indicando claramente su polaridad.


2,5 puntos

- a) This is a network with 2 junctions and two loops, and so we'll need one equation for junctions and two equations for loops:

$$\left. \begin{aligned} I_1 - I_2 + I_3 &= 0 \\ V_{AD} = 96 &= I_1 \cdot 6 - I_3 \cdot 3 - (-60) \\ V_{CD} = 48 &= -I_2 \cdot 6 - I_3 \cdot 3 - (-60) \end{aligned} \right\} \Rightarrow I_1 = 5 \text{ A} \quad I_2 = 3 \text{ A} \quad I_3 = -2 \text{ A}$$

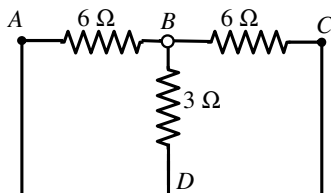- b)  $V_B - V_D = -3I_3 - (-60) = -3(-2) + 60 = 66$  V

Passive circuit and equivalent resistance between B and D (removing all the generators) are:



$$\frac{1}{R_{eq}} = \frac{1}{6} + \frac{1}{6} + \frac{1}{3} \Rightarrow R_{eq} = 1,5 \Omega$$

So, Thevenin's equivalent generator between B and D will be:

