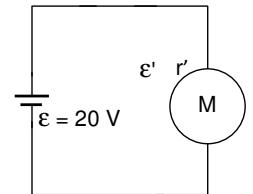




1. (3 points) On circuit on picture, the motor is fed by an **ideal generator** with electromotive force $\epsilon=20\text{ V}$. The consumed power by the motor is $P_c=40\text{ w}$ and its efficiency **80 %**. Calculate:
- (0,6) The power supplied by the generator to the circuit, P_s .
 - (0,6) The intensity of current of circuit, I , giving the **polarity of motor** (terminals positive and negative).
 - (0,6) The turned power by the motor into mechanical energy, P_t and that consumed on its internal resistance P_r .
 - (0,6) The contraelectromotive force ϵ' of motor and its internal resistance r' .
 - (0,6) If the **internal resistance of motor** was null, ¿which would be its **efficiency**?


1. (3 puntos) En el circuito de la figura, el motor está alimentado por un **generador ideal** de f.e.m. $\epsilon=20\text{ V}$. La potencia consumida por el motor es $P_c=40\text{ w}$ y su rendimiento del **80 %**. Calcular:
- (0,6) La potencia suministrada por el generador al circuito, P_s .
 - (0,6) La intensidad de corriente del circuito, I , indicando la **polaridad del motor** (terminales positivo y negativo).
 - (0,6) La potencia transformada por el motor en energía mecánica, P_t y la consumida en su resistencia interna P_r .
 - (0,6) La f.c.e.m. ϵ' y la resistencia interna r' del motor.
 - (0,6) Si la **resistencia interna del motor** fuera nula, ¿cuál sería su **rendimiento**?



- As there only are on circuit generator and motor, all the consumed power on motor must be supplied by the generator. Therefore: $P_s = P_c = 40\text{ w}$
- As generator is ideal, generated power equals supplied power. Therefore $P_g = \epsilon I = 40 \Rightarrow I = \frac{40}{\epsilon} = \frac{40}{20} = 2\text{ A}$
Clockwise direction. Upper terminal of motor is the positive terminal, and lower terminal is the negative one.
- $\eta = \frac{P_t}{P_c} \Rightarrow 0,8 = \frac{P_t}{40} \Rightarrow P_t = 40 \cdot 0,8 = 32\text{ w}$ $P_r = P_c - P_t = 40 - 32 = 8\text{ w}$
- $P_r = \epsilon' I = 32 \Rightarrow \epsilon' = \frac{32}{I} = \frac{32}{2} = 16\text{ V}$ $P_r = I^2 r' = 8 \Rightarrow r' = \frac{8}{I^2} = \frac{8}{4} = 2\ \Omega$
- If internal resistance of motor is null, $P_r = 0$ and then $P_c = P_t$ Therefore $\eta = \frac{P_t}{P_c} = 1$


2. (3 points) Given the circuit on picture, compute:
- (1,2) Intensity of current flowing along each branch with the shown directions, I_1 , I_2 and I_3 .
 - (0,6) **Potential** of point **B**.
 - (0,6) **Thevenin's equivalent generator** between points **B** and **D**, clearly showing its polarity.
 - (0,6) **Thevenin's equivalent generator** between points **A** and **D**, clearly showing its polarity.

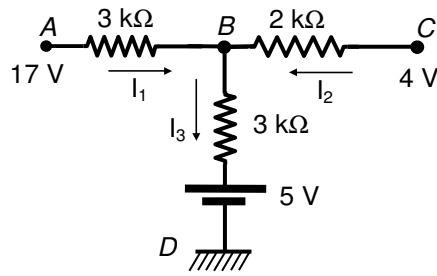2. (3 puntos) Dado el circuito de la figura, calcula:
- (1,2) La intensidad de corriente en cada rama con los sentidos mostrados, I_1 , I_2 y I_3 .
 - (0,6) **Potencial** del punto **B**.
 - (0,6) El **generador equivalente de Thevenin** entre los puntos **B** y **D**, indicando claramente su polaridad.
 - (0,6) El **generador equivalente de Thevenin** entre los puntos **A** y **D**, indicando claramente su polaridad.




This is a network with 2 junctions and two loops, and so we'll need one equation for junctions and two equations for loops:

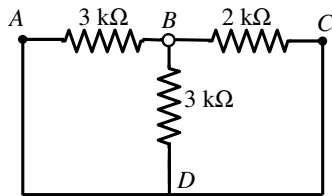- $$I_1 + I_2 = I_3$$
- a)
$$\left. \begin{aligned} V_{AD} = 17 &= 3I_1 + 3I_3 - (-5) \\ V_{CD} = 4 &= 2I_2 + 3I_3 - (-5) \end{aligned} \right\} \Rightarrow I_1 = 3 \text{ mA} \quad I_2 = -2 \text{ mA} \quad I_3 = 1 \text{ mA}$$
- b)
$$V_B = V_B - V_D = 3I_3 - (-5) = 3 \cdot 1 + 5 = 8 \text{ V}$$
- c) Passive circuit and equivalent resistance between B and D (removing all the generators) is



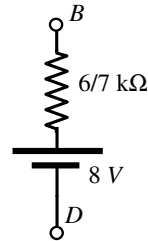
$$\frac{1}{R_{eqBD}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{2} \Rightarrow R_{eqBD} = \frac{6}{7} \text{ k}\Omega$$



So, Thevenin's equivalent generator between B and D is:

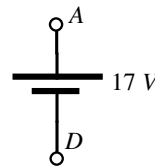d)
$$V_A - V_D = 17 \text{ V} \quad R_{eqAD} = 0$$

So, Thevenin's equivalent generator between A and D is:




3. (2 points) The picture shows a square loop (sides 1, 2, 3 and 4) with side **a** flowed by an intensity of current **I**. The loop lies on plane **XY** and it's placed inside a uniform magnetic field $\vec{B} = B_0 \vec{j}$. Compute:

- (0,6) The **force** acting on **each side** of loop. Give the results in **vector form**.
- (0,4) The **total force** acting on loop.
- (0,5) The **magnetic moment** of loop.
- (0,5) The **torque** acting over the loop.

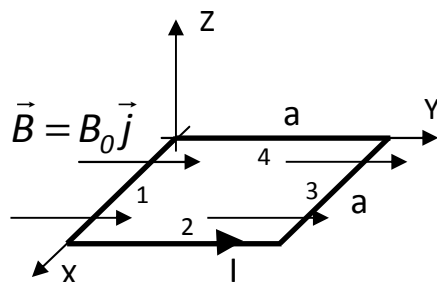3. (2 puntos) La figura muestra una espira cuadrada (lados 1, 2, 3 y 4) de lado **a** y por la que circula una corriente **I**. La espira está situada en el plano **XY**, dentro de un campo magnético uniforme $\vec{B} = B_0 \vec{j}$. Calcula:

- (0,6) La **fuerza** que actúa sobre **cada uno de los lados** de la espira. Da el resultado en **forma vectorial**.
- (0,4) La **fuerza total** que actúa sobre la espira.
- (0,5) El **momento magnético** de la espira.
- (0,5) El **par (momento)** que actúa sobre la espira.



$$a) \vec{F}_1 = I a \vec{i} \times B_0 \vec{j} = I a B_0 \vec{k} \quad \vec{F}_3 = I (-a \vec{i}) \times B_0 \vec{j} = -I a B_0 \vec{k} \quad \vec{F}_2 = \vec{F}_4 = 0$$

$$b) \text{ The total force acting on a loop inside a uniform magnetic field is zero. } \vec{F}_{TOT} = \sum_{i=1,4} \vec{F}_i = 0$$

$$c) \text{ As we only have one loop: } \vec{\mu} = I \vec{S} = I a^2 \vec{k}$$


$$d) \vec{\tau} = \vec{\mu} \times \vec{B} = I a^2 \vec{k} \times B_0 \vec{j} = -I a^2 B_0 \vec{i}$$

4. (2 points) An infinite straight carrying current conductor lies over **X** axis, flowing an intensity **I** along it. A circular loop, flowed by the same intensity **I** is placed on plane **XY** with its centre at point **(2,2,0) m**. Radius of circular loop is **1 m**. The **directions** of both intensities are those shown on picture. Calculate:

- a) (1) The **total magnetic field** at the **centre** of circular loop (point O). Give the result as a **vector**, as a function of μ_0 and I .
- b) (0,5) An electron (charge $-q$) is released at the centre of circular loop with velocity $\vec{v} = v_0 \vec{j}$. Calculate the **vector force** acting on such electron. Give the result as a function of q , v_0 , μ_0 and I .
- c) (0,5) If we add a new infinite straight carrying current conductor lying along **Y** axis, ¿which should be the intensity along this conductor in order the total **magnetic field** at the **centre** of circular loop was **zero**? Give the **direction** of such intensity (positive or negative direction of Y axis) explaining **why**.

4. (2 puntos) Un conductor rectilíneo infinito está situado a lo largo del eje **X**, y lleva una corriente **I**. Una espira circular conduce la misma corriente **I**, y está situada en el plano **XY** con su centro en el punto **(2,2,0) m**. Su radio es de **1 m**. Las **direcciones** de ambas intensidades se pueden ver en el dibujo. Calcula:

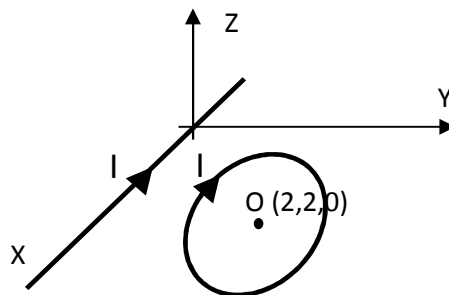- a) (1) El **campo magnético total** en el **centro** de la espira circular (punto O). Expresa el resultado en forma **vectorial** en función de μ_0 e I .
- b) (0,5) Un electrón (carga $-q$) es liberado en el centro de la espira circular con velocidad $\vec{v} = v_0 \vec{j}$. Calcula el **vector fuerza** que actúa sobre el electrón. Expresa el resultado en función de q , v_0 , μ_0 e I .
- c) (0,5) Si añadimos un nuevo conductor rectilíneo e infinito colocado sobre el eje **Y**, ¿cuál debería ser la corriente que circulara por dicho conductor para que el **campo magnético total** en el **centro** de la espira circular sea **cero**? Da la **dirección** de dicha corriente (dirección positiva o negativa del eje Y) explicando **porqué**.



$$a) \vec{B} = -\frac{\mu_0 I}{2\pi \cdot 2} \vec{k} - \frac{\mu_0 I}{2 \cdot 1} \vec{k} = -\frac{\mu_0 I}{2} \left(\frac{1}{2\pi} + 1 \right) \vec{k}$$

$$b) \vec{F} = -q \vec{v} \times \vec{B} = -q v_0 \vec{j} \times \left(-\frac{\mu_0 I}{2} \left(\frac{1}{2\pi} + 1 \right) \vec{k} \right) = \frac{q v_0 \mu_0 I}{2} \left(\frac{1}{2\pi} + 1 \right) \vec{i}$$

- c) If we add a new infinite straight carrying current conductor along Y axis, being I' the intensity flowing along it, the magnetic field created by this conductor would be (in modulus): $B' = \frac{\mu_0 I'}{2\pi \cdot 2} = \frac{\mu_0 I'}{4\pi}$

This magnetic field should go in the positive direction of Z axis, because the magnetic field calculated on paragraph a) goes in the negative direction of Z axis. For this reason, I' should flow in the negative direction of Y axis. And to obtain null total magnetic field must be verified that

$$\frac{\mu_0 I}{2} \left(\frac{1}{2\pi} + 1 \right) = \frac{\mu_0 I'}{4\pi} \Rightarrow I' = (1 + 2\pi) I$$

FORM

Direct current $V_A - V_B = I \sum R - \sum \mathcal{E}$ $I = \frac{\sum \mathcal{E}}{\sum R}$ $P = V \cdot I$ $\mathcal{E} = \frac{dW}{dq}$ $P_R = I^2 \cdot R$

$P_g = \mathcal{E} \cdot I$ $P_t = \mathcal{E}' \cdot I$ $P_g - P_r = P_s$ $P_t + P_{r'} = P_c$ $\eta_g = \frac{P_s}{P_g}$ $\eta_r = \frac{P_t}{P_c}$

Magnetic Forces $\vec{F} = q(\vec{v} \times \vec{B})$ $d\vec{F} = Id\vec{l} \times \vec{B}$ $\vec{\mu} = N \cdot I \cdot \vec{S}$ $\vec{\tau} = \vec{\mu} \times \vec{B}$ $V_H = \frac{I \cdot B \cdot d}{n \cdot e \cdot S}$

Sources of magnetic field $d\vec{B} = \frac{\mu_0 I}{4\pi} \frac{d\vec{l} \times \vec{r}}{r^3}$ $\mu_0 = 4\pi 10^{-7} \text{ (I.S. units)}$ $B = \frac{\mu_0 I}{2\pi x}$

$B = \frac{\mu_0 I}{2R}$ $\oint_L \vec{B} \cdot d\vec{l} = \mu_0 \sum I$ $B = \frac{\mu_0 NI}{l}$