



1. (2,5) Two point charges of $2 \mu\text{C}$ and $-4 \mu\text{C}$ are placed on vacuum at points A(0,3) m and B(0,-8) m.

a) (1) Find the total electric field at point C(-4,0) m. Draw this total electric field and also the electric field vector created by each charge.

b) (0,8) Compute the work done by the electric field to move a $-3 \mu\text{C}$ point charge from the infinite to point C. ¿Who's doing this work (the field or some force external to the field)?

c) (0,7) Find a point lying on Y axis between points A and B where the electric potential was zero.


1. (2,5) Dos cargas puntuales de $2 \mu\text{C}$ y $-4 \mu\text{C}$ se encuentran en el vacío en las posiciones A(0,3) m y B(0,-8) m respectivamente.

a) (1) Calcula el campo eléctrico resultante en el punto C(-4,0) m. Dibuja los vectores campo eléctrico que crea cada carga y el campo eléctrico resultante.

b) (0,8) Calcula el trabajo realizado por el campo eléctrico al desplazar una carga de $-3 \mu\text{C}$ desde el infinito al punto C. ¿Quién realiza el trabajo?

c) (0,7) Halla un punto entre A y B (en el eje OY) en el que el potencial sea cero.

a)

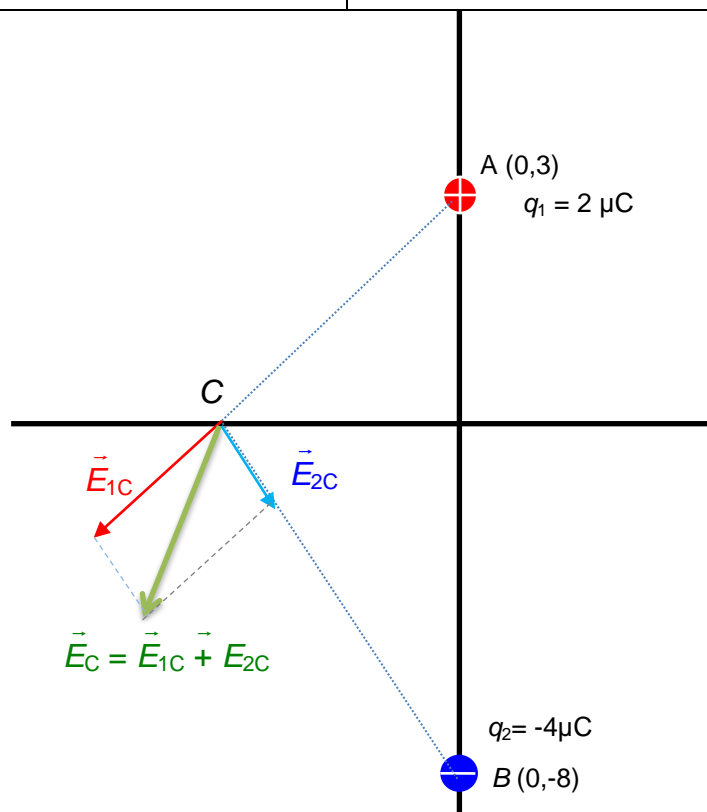

0,3 points

$$\vec{E}_{1C} = K \frac{q_1}{r_1^2} \vec{u}_{r,1} = 9 \cdot 10^9 \frac{2 \cdot 10^{-6}}{5^2} \left(\frac{-4\vec{i} - 3\vec{j}}{5} \right) = (-576\vec{i} - 432\vec{j}) \text{ (N/C)}$$

0.6 points

$$\vec{E}_{2C} = K \frac{q_2}{r_2^2} \vec{u}_{r,2} = 9 \cdot 10^9 \frac{4 \cdot 10^{-6}}{80} \left(\frac{4\vec{i} - 8\vec{j}}{\sqrt{80}} \right) = (201,25\vec{i} - 402,4\vec{j}) \text{ (N/C)}$$

0.1 points

$$\vec{E}_C = \vec{E}_{1C} + \vec{E}_{2C} = (-374,8\vec{i} - 834,4\vec{j}) \text{ (N/C)}$$

b) $V_{1C} = K \frac{q_1}{r_1} = 9 \cdot 10^9 \frac{2 \cdot 10^{-6}}{5} = 3600 \text{ V}$

$$V_{2C} = K \frac{q_2}{r_2} = 9 \cdot 10^9 \frac{-4 \cdot 10^{-6}}{\sqrt{80}} = -4024,9 \text{ V}$$

$$V_C = V_{1C} + V_{2C} = -424,9 \text{ V}$$

0,4 points

$$W_{\infty C} = q(V_{\infty} - V_C) = -3 \cdot 10^{-6}(0 - (-424,9)) = -1,274 \cdot 10^{-3} \text{ J}$$

0,2 points

The negative sign is telling us that the work to carry the charge from infinite to point C is done by external forces.

0,2 points

c) We are looking for a point P in such way that

$$V_P = V_{1P} + V_{2P} = 0 \text{ V} \quad \text{being} \quad V_P = k \frac{q_1}{r_{1P}} + k \frac{q_2}{r_{2P}} = 0 \text{ V}$$

Let us call y the distance of such point to point A. Therefore:

$$\frac{2}{y} = \frac{4}{(11-y)} \Rightarrow y = 3,66 \text{ m} \quad \text{then, point P is } P(0, -0,66) \text{ m}$$

0,7 points

2. (2,5) State Gauss's law (1,2) and apply it to calculate the electric field created by an spherical conductor charged with a charge Q:

- a) (0,7) At a distance $2R$ from its centre
- b) (0,6) At a distance $R/2$ from its centre

2. (2,5) Enuncia el teorema de Gauss (1,2) y aplícalo para calcular el campo eléctrico creado por un conductor esférico cargado con una carga Q:

- a) (0,7) A una distancia $2R$ de su centro
- b) (0,6) A una distancia $R/2$ de su centro

Gauss's law:

The flux of the electric field through a closed surface S equals the enclosed charge inside such surface divided into the dielectric permittivity.

1,2 points

a) On first we choose a spherical surface with radius $2R$, concentric with the charged surface. At any point of such surface electric field and surface vector are parallel and the modulus of electric field is constant. Therefore:

$$\Phi = \oint_S \vec{E} \cdot d\vec{S} = \oint_S E \cdot dS = E \oint_S dS = E \cdot 4\pi(2R)^2 = \frac{Q}{\epsilon_0} \quad \Rightarrow \quad E = \frac{Q}{16\pi\epsilon_0 R^2}$$

0,7 points

b) As we have done above:

$$\Phi = \oint_S \vec{E} \cdot d\vec{S} = \frac{Q}{\epsilon_0}$$

Now, as we are inside a charged conductor in equilibrium, the volumetric density of charge is null, there is no charge inside the conductor, and every charges are over its Surface. So, the flux of the electric field through the spherical surface of radius $R/2$ is null and also the electric field.


0,6 points

3. (2,5) The picture shows 3 equal capacitors with capacitance C each, connected to a difference of potential V .

- a) (1,2) Find the charge on each capacitor and the difference of potential on terminals of each one.
- b) (1,3) The battery is removed and a dielectric with relative permittivity $\epsilon_r=4$ is introduced on capacitor 1. Find the new charge on each capacitor and the difference of potential on terminals of each one.

3. (2,5) La figura muestra 3 condensadores iguales de capacidad C , conectados a una diferencia de potencial V .

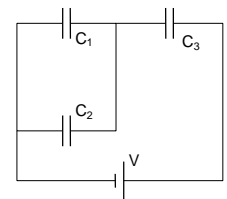- a) (1,2) Halla la carga en cada condensador y la d.d.p. en bornes de cada condensador.
- b) (1,3) Se retira la fuente y se introduce un dieléctrico de permitividad relativa $\epsilon_r=4$ en el condensador 1. Halla la nueva carga en cada condensador y la d.d.p. en bornes de cada condensador.




a) The equivalent capacitance of capacitors C_1 and C_2 in parallel is

$$C_{1,2} = \sum_{i=1}^n C_i = C_1 + C_2 = C + C = 2C$$

Capacitors $C_{1,2}$ and C_3 are connected in series; so, the equivalent capacitance of this set is:
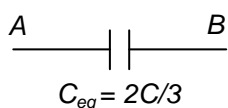
$$\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i} = \frac{1}{C_{1,2}} + \frac{1}{C_3} = \frac{1}{2C} + \frac{1}{C} = \frac{1}{2C} + \frac{2}{2C} = \frac{3}{2C} \Rightarrow C_{eq} = \frac{2C}{3}$$



The total charge of system when a difference of potential V is applied is:

$$Q_T = C_{eq}V = \frac{2}{3}CV$$

0,2 points

Both capacitors C_3 y $C_{1,2}$ have equal charges, it is: $Q_T = Q_3 = Q_{1,2} = \frac{2}{3}CV$

$$Q_T = Q_1 + Q_2 = \frac{2}{3}CV \text{ and } Q_1 = Q_2 = \frac{1}{3}CV$$

0,5 points

$$V_1 = V_2 = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_{1,2}}{C_{1,2}} = \frac{1}{3}V$$

0,5 points

$$V_3 = \frac{Q_3}{C_3} = \frac{2}{3}V$$

b) When the battery is disconnected, the total charge of set remains constant, and when the dielectric is introduced on C_1 , the new equivalent capacitance is:

$$C_{1,2} = \sum_{i=1}^n C_i = C_1 + C_2 = 4C + C = 5C$$

$$\frac{1}{C_{eq}} = \sum_{i=1}^n \frac{1}{C_i} = \frac{1}{C_{1,2}} + \frac{1}{C_3} = \frac{1}{5C} + \frac{1}{C} = \frac{6}{5C} \Rightarrow C_{eq} = \frac{5}{6}C$$

0,1 points

$$Q_T = \frac{2}{3}CV \quad Q_T = Q_3 = Q_{1,2} = \frac{2}{3}CV$$

$$Q_T = Q_1 + Q_2 = \frac{2}{3}CV$$

0,2 points

Capacitors 1 and 2 are connected in parallel to the same d.d.p. Therefore:

$$\frac{Q_1}{4C_1} = \frac{Q_2}{C_2} \quad \frac{Q_1}{4C} = \frac{Q_2}{C}, \text{ and } Q_1 = 2Q_2 \quad Q_1 = \frac{8}{15}CV \quad Q_2 = \frac{2}{15}CV$$

0,5 points

Voltages on terminals of each capacitor will be:

$$V_1 = V_2 = \frac{Q_1}{C_1} = \frac{Q_2}{C_2} = \frac{Q_{1,2}}{C_{1,2}} = \frac{2}{15}V$$

0,5 points

$$V_3 = \frac{Q_3}{C_3} = \frac{2}{3}V$$

4. (2,5) On the association of resistors of the picture, is known that $V_{BD} = 4 \text{ V}$.


Compute:

- (1,5) $I_1, I_2, I_3, I, V_{CD}, V_{BC}, V_{AB}$ and V_{AD} .
- (0,5) Equivalent resistance between points A and D
- (0,5) Equivalent resistance between points A and C

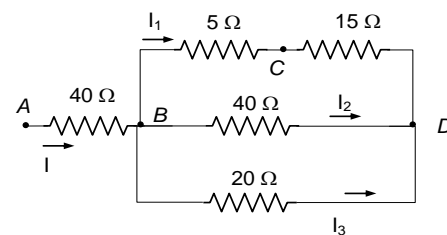4. (2,5) En la asociación de resistencias de la figura, se sabe que $V_{BD} = 4 \text{ V}$.

Calcula:

- (1,5) $I_1, I_2, I_3, I, V_{CD}, V_{BC}, V_{AB}$ y V_{AD} .
- (0,5) Resistencia equivalente entre A y D
- (0,5) Resistencia equivalente entre A y C



By applying Ohm's law to 40Ω resistor:

$$V_{BD} = 4 = I_2 \cdot 40 \Rightarrow I_2 = \frac{4}{40} = 0,1 \text{ A}$$

$$V_{BD} = 4 = I_3 \cdot 20 \Rightarrow I_3 = \frac{4}{20} = 0,2 \text{ A}$$

$$V_{BD} = 4 = I_1 \cdot 20 \Rightarrow I_1 = \frac{4}{20} = 0,2 \text{ A}$$

$$I = I_1 + I_2 + I_3 = 0,5 \text{ A}$$

$$\text{So } V_{BC} = 5 \cdot I_1 = 5 \cdot 0,2 = 1 \text{ V}$$

$$V_{CD} = 15 \cdot 0,2 = 3 \text{ V}$$

$$V_{AB} = 5 \cdot I_1 = 40 \cdot 0,5 = 20 \text{ V}$$

0,8 points

$$V_{AD} = V_{AB} + V_{BD} = 20 + 4 = 24 \text{ V}$$

0,7 points

Equivalent resistance between A and D







$$R_{eqAD} = 40 + \left(\frac{1}{20} + \frac{1}{40} + \frac{1}{20} \right)^{-1} = 40 + 8 = 48 \text{ } \Omega$$

0,5 points

Equivalent resistance between A and C

$$R_{eqAC} = 40 + 4,31 = 44,31 \text{ } \Omega$$

0,5 points

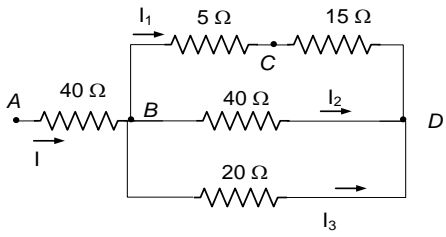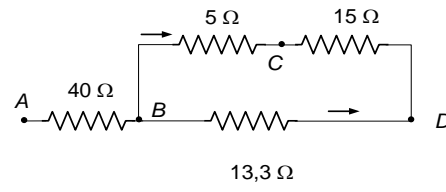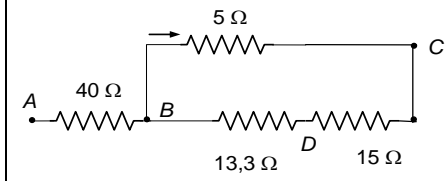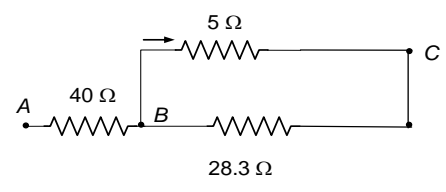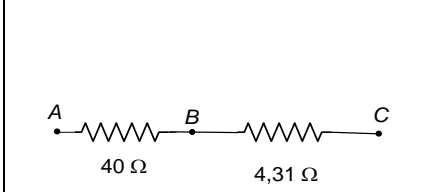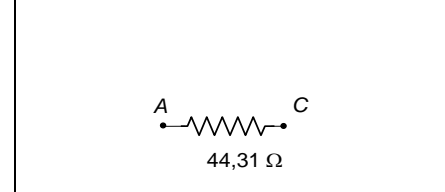 $R_{40,20} = \left(\frac{1}{20} + \frac{1}{40} \right)^{-1} = 13,3 \text{ } \Omega$	 $R_{13,3-15} = 13,30 + 15 = 28,3 \Omega$	
 $R_{5,28,3} = \left(\frac{1}{5} + \frac{1}{28,3} \right)^{-1} = 4,31 \text{ } \Omega$	 $R_{eqAC} = 40 + 4,31 = 44,31 \text{ } \Omega$	

Si te examinas sólo de una parte, debes resolver los cuatro problemas de esa parte.

If you are sitting only one part of the exam, then you have to solve the four problems of that part.

Si te examinas de dos partes, debes resolver los tres primeros problemas de ambas partes.

If you are sitting two parts of the exam, then you have to solve the three first problems of both parts.

Si te examinas de las tres partes, debes resolver los dos primeros problemas de cada una de las partes.

If you are sitting the three parts of the exam, then you have to solve the two first problems of every part.

Form on rear side – Fórmulas en la parte de atrás

Form - Fórmulas

Electrostatics

$$\vec{F} = K \frac{q_1 q_2}{r^2} \vec{u}_r \quad \vec{E} = \frac{\vec{F}}{q} \quad K = \frac{1}{4\pi\epsilon_0} = 9 \cdot 10^9 \text{ (S.I.)} \quad V_A - V_B = \int_A^B \vec{E} \cdot d\vec{r}$$

$$\vec{E} = K \frac{q}{r^2} \vec{u}_r \quad V = K \frac{q}{r} \quad \int_S \vec{E} \cdot d\vec{S} = \frac{\sum Q}{\epsilon_0} \quad W_{AB} = q(V_A - V_B)$$

Conductors and capacitors

$$E = \frac{\sigma}{\epsilon_0} \quad C = \frac{Q}{V} \quad C = \frac{\epsilon_0 S}{d}$$

$$C_{eq} = \sum C_i \quad \frac{1}{C_{eq}} = \sum \frac{1}{C_i} \quad E_d = \frac{E}{\epsilon_r} \quad C_d = \epsilon_r C \quad W = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{V^2 C}{2}$$

Direct Current

$$\vec{J} = n \cdot e \cdot \vec{v}_a \quad \vec{J} = \sigma \cdot \vec{E} \quad R = \frac{V_1 - V_2}{I} \quad R = \rho \frac{L}{S}$$

$$\rho = \rho_0(1 + \alpha(T - T_0)) \quad P_R = IV = I^2 R = \frac{V^2}{R}$$