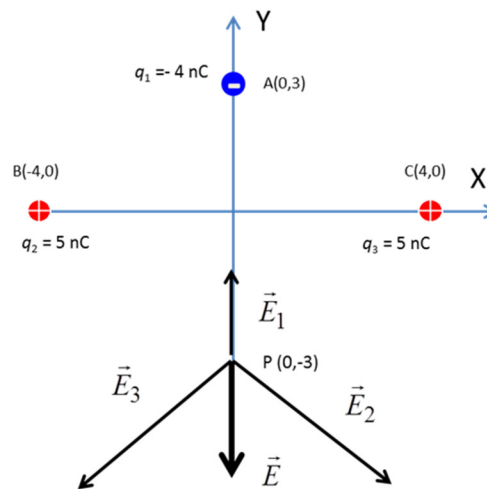




- 1. (3 points)** Given the **three point charges** on picture:
- Compute the **electric field** vector at point **P** due to the three charges. Draw the electric field created by each charge at P and the total electric field.
 - Compute the **work** needed to carry a **2 μC** charge **from point P** up to the **origin of coordinates**. Is this work done by the forces of the electric field or against them?
 - ¿What **point of the Y axis** should the charge **q₁** moved to (q₂ and q₃ remain unmoved) in order the **potencial** at the **origin** of coordinates was **null**?

- 1. (3 puntos)** Dadas las **tres cargas** puntuales de la figura:
- Calcula el vector **campo eléctrico** en el punto **P** debido a las tres cargas. Dibuja el campo que crea cada carga en P y el campo resultante.
 - Calcula el **trabajo** necesario para llevar una carga de **2 μC desde el punto P** hasta el **origen de coordenadas**. Este trabajo ¿es hecho por las fuerzas del campo, o en contra de ellas?
 - ¿A qué **punto del eje Y** deberíamos mover la carga **q₁** (q₂ y q₃ permanecen en los mismos puntos) para que el **potencial** en el **origen** de coordenadas **se anule**?



$$\text{a) } \vec{E}_1 = k \frac{q_1 \vec{j}}{r^2} = \frac{9 \cdot 10^9 \cdot 4 \cdot 10^{-9}}{6^2} \vec{j} = \vec{j} \text{ N/C}$$

$$\vec{E}_2 = k \frac{q_2}{r^2} \left(\frac{4\vec{i} - 3\vec{j}}{5} \right) = \frac{9 \cdot 10^9 \cdot 5 \cdot 10^{-9}}{5^2} \left(\frac{4\vec{i} - 3\vec{j}}{5} \right) = \frac{9}{25} (4\vec{i} - 3\vec{j}) \text{ N/C} \quad \vec{E}_3 = \frac{9}{25} (-4\vec{i} - 3\vec{j}) \text{ N/C}$$

$$\vec{E} = \vec{E}_1 + \vec{E}_2 + \vec{E}_3 = \vec{j} + \frac{9}{25} (4\vec{i} - 3\vec{j}) + \frac{9}{25} (-4\vec{i} - 3\vec{j}) = \vec{j} - 2 \frac{27}{25} \vec{j} = -\frac{29}{25} \vec{j} \text{ N/C}$$

$$\text{b) } V_{P1} = k \frac{q_1}{d_1} = \frac{9 \cdot 10^9 (-4 \cdot 10^{-9})}{6} = -6 \text{ V} \quad V_{P2} = k \frac{q_2}{d_2} = \frac{9 \cdot 10^9 \cdot 5 \cdot 10^{-9}}{5} = 9 \text{ V} = V_{P3}$$

$$V_P = V_{P1} + V_{P2} + V_{P3} = -6 + 9 + 9 = 12 \text{ V}$$

$$V_{O1} = k \frac{q_1}{d_1} = \frac{9 \cdot 10^9 (-4 \cdot 10^{-9})}{3} = -12 \text{ V} \quad V_{O2} = k \frac{q_2}{d_2} = \frac{9 \cdot 10^9 \cdot 5 \cdot 10^{-9}}{4} = \frac{45}{4} \text{ V} = V_{O3}$$

$$V_O = V_{O1} + V_{O2} + V_{O3} = -12 + 2 \frac{45}{4} = \frac{21}{2} \text{ V}$$

$$W = q(V_P - V_O) = 2 \cdot 10^{-6} \left(12 - \frac{21}{2} \right) = 3 \cdot 10^{-6} \text{ J} \quad \text{As this work is positive, it's done by the forces of the electric field.}$$

- c)** If we move the charge **q₁** to point (0,y) and the electric potential at point O must be null, then must be verified that:

$$0 = \frac{9 \cdot 10^9 (-4 \cdot 10^{-9})}{y} + 2 \frac{9 \cdot 10^9 (5 \cdot 10^{-9})}{4} \Rightarrow \frac{4}{y} = \frac{5}{2} \Rightarrow y = \frac{8}{5} \text{ m}$$

So, the point to move **q₁** is (0,8/5) m. Obviously, point (0,-8/5) m is also a solution.

| | |
|--|--|
| <p>2. (2 points) State Gauss's law and apply it to calculate the electric field created by a spherical conductor with radius R and charged with charge Q:</p> <p>a) At a distance 3R from its centre.</p> <p>b) At a distance R/3 from its centre.</p> | <p>2. (2 puntos) Enuncia el teorema de Gauss y aplícalo para calcular el campo eléctrico creado por un conductor esférico de radio R cargado con carga Q:</p> <p>a) A una distancia 3R de su centro.</p> <p>b) A una distancia R/3 de su centro.</p> |
|--|--|



Gauss's law: The net outward flux through any closed surface equals the net charge inside the surface divided by ϵ_0

- a) Let's consider a spherical surface with radius $3R$. At any point of such Surface, electric field and Surface vector are parallel. According Gauss's law, the electric flux trough such surface is

$$\phi = \int_{\text{Sphere}} \vec{E} d\vec{S} = \int_{\text{Sphere}} E dS = E 4\pi (3R)^2 = \frac{Q}{\epsilon_0} \Rightarrow E = \frac{Q}{36\pi\epsilon_0 R^2}$$

- b) Let's consider a spherical surface with radius $R/3$. According Gauss's law, and taking in account that there isn't any charge inside such surface $\phi = \int_{\text{Sphere}} \vec{E} d\vec{S} = \int_{\text{Sphere}} E dS = E 4\pi (R/3)^2 = \frac{0}{\epsilon_0} \Rightarrow E = 0$

| | |
|--|---|
| <p>3. (2,5 points) The association of capacitors on picture is connected to a difference of potential $V_A - V_F = 10 \text{ V}$</p> <p>a) Compute the charge on each capacitor (Q_1, Q_2, Q_3 and Q_4) and the difference of potential between their terminals (V_1, V_2, V_3 and V_4).</p> <p>b) The distance between plates of capacitor C_3 is reduced to a half and a dielectric having relative dielectric permittivity $\epsilon_r = 2$ is inserted between the plates of capacitor C_1. Compute the new equivalent capacitance of the set between terminals A and F.</p> <p>c) With the conditions given on a), point F is linked to ground. Give the electric potential of points B and D.</p> | <p>3. (2,5 puntos) La asociación de condensadores de la figura se conecta a una d.d.p. $V_A - V_F = 10 \text{ V}$</p> <p>a) Calcula la carga en cada condensador (Q_1, Q_2, Q_3 y Q_4) y la diferencia de potencial entre sus terminales (V_1, V_2, V_3 y V_4).</p> <p>b) La distancia entre las placas del condensador C_3 se reduce a la mitad y se introduce un dieléctrico de permitividad dieléctrica relativa $\epsilon_r = 2$ entre las placas del condensador C_1. Calcula la nueva capacidad equivalente del conjunto entre los terminales A y F.</p> <p>c) Manteniendo las condiciones dadas en a), el punto F se conecta a tierra. ¿Cuál es el potencial eléctrico de los puntos B y D?</p> |
|--|---|

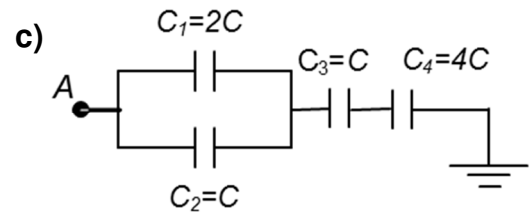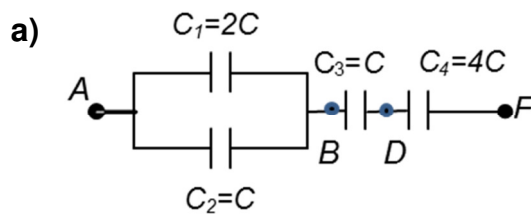

- a) This exercise can be solved in two different ways. Both are correct:
- Without calculating the equivalent capacitance of the association:
 - Capacitors 1 and 2 are connected in parallel and then $V_1 = V_2 \Rightarrow \frac{Q_1}{2C} = \frac{Q_2}{C} \Rightarrow Q_1 = 2Q_2$
 - Capacitors 3 and 4 are connected in series and then $Q_3 = Q_4$
 - The charge of capacitor 3 is divided among the plates of capacitors 1 and 2 and then:

$$Q_1 + Q_2 = Q_3 \Rightarrow Q_1 = \frac{2Q_3}{3}$$
 - The difference of potential between A and B equals 10 V: $V_1 + V_3 + V_4 = \frac{Q_1}{2C} + \frac{Q_3}{C} + \frac{Q_4}{4C} = 10$
- From the before equations, we have four equations with four unknowns, and every Q and V can be solved:
- $$\frac{2Q_3}{6C} + \frac{Q_3}{C} + \frac{Q_3}{4C} = 10 \Rightarrow Q_3 = Q_4 = \frac{12}{19} C \cdot 10 = \frac{120}{19} C \Rightarrow Q_1 = \frac{80}{19} C \text{ and } Q_2 = \frac{40}{19} C$$
- $$V_1 = V_2 = \frac{Q_1}{2C} = \frac{40}{19} V \quad V_3 = \frac{Q_3}{C} = \frac{120}{19} V \quad V_4 = \frac{Q_4}{4C} = \frac{30}{19} V$$
- Obviously it is verified that $V_1 + V_3 + V_4 = \frac{40}{19} + \frac{120}{19} + \frac{30}{19} = \frac{190}{19} = 10 \text{ V}$
- By using the equivalent capacitance of the set of capacitors. 1 and 2 are in parallel and then $C_{12} = 2C + C = 3C$. C_{12} is in series with C_3 and C_4 . Therefore

$$\frac{1}{C_{eq}} = \frac{1}{C_{12}} + \frac{1}{C_3} + \frac{1}{C_4} = \frac{1}{3C} + \frac{1}{C} + \frac{1}{4C} = \frac{19}{12C} \Rightarrow C_{eq} = \frac{12}{19}C$$

The charge of the equivalent capacitor equals the charge of C_4 and then $Q_4 = Q_3 = C_{eq} \cdot 10 = \frac{12}{19}C \cdot 10 = \frac{120}{19}C$

$$V_3 = \frac{Q_3}{C} = \frac{120}{19}V \quad V_4 = \frac{Q_4}{4C} = \frac{30}{19}V \quad V_1 = V_2 = 10 - (V_3 + V_4) = 10 - \left(\frac{120}{19} + \frac{30}{19}\right) = \frac{40}{19}V$$

$$Q_1 = 2CV_1 = \frac{80}{19}C \quad Q_2 = CV_2 = \frac{40}{19}C$$

b) With the new conditions, $C'_1 = 4C$ and $C'_3 = 2C$. Therefore, the new equivalent capacitance is:

$$\frac{1}{C'_{eq}} = \frac{1}{5C} + \frac{1}{2C} + \frac{1}{4C} = \frac{19}{20C} \Rightarrow C'_{eq} = \frac{20}{19}C$$

c) If point F is linked to ground, then its potential is zero and potential of point A is 10 V. Therefore

$$V_B = V_A - V_1 = 10 - \frac{40}{19} = \frac{150}{19}V \quad \text{and} \quad V_D = V_B - V_3 = \frac{150}{19} - \frac{120}{19} = \frac{30}{19}V \quad \text{Obviously, } V_D = V_4$$

4. (2,5 points) Given the association of resistors on picture, it is known that $V_{AB} = 10$ V.


Find:

- $I_1, I_2, I_3, I, V_{CD}, V_{BD}, V_{BC}$ and V_{AD} .
- The equivalent resistance between points A and D.
- The equivalent resistance between points A and C.

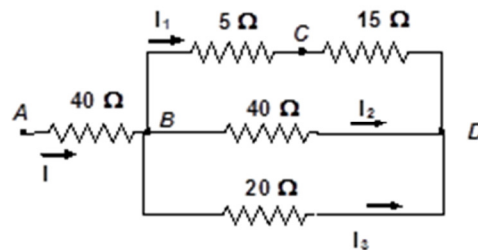4. (2,5 puntos) En la asociación de resistencias de la figura, se sabe que $V_{AB} = 10$ V.

Calcula:

- $I_1, I_2, I_3, I, V_{CD}, V_{BD}, V_{BC}$ y V_{AD} .
- Resistencia equivalente entre A y D.
- Resistencia equivalente entre A y C.



$$\text{a) } I = \frac{V_{AB}}{40} = \frac{10}{40} = \frac{1}{4}A \quad V_{BD} = I_1(5+15) = I_2 \cdot 40 = I_3 \cdot 20 \Rightarrow I_3 = 2I_2 \quad \text{and} \quad I_1 = 2I_2$$


$$\text{Moreover } I = I_1 + I_2 + I_3 \Rightarrow \frac{1}{4} = 2I_2 + I_2 + 2I_2 = 5I_2 \Rightarrow I_2 = \frac{1}{20}A \quad I_1 = \frac{1}{10}A \quad I_3 = \frac{1}{10}A$$

$$V_{BD} = I_2 \cdot 40 = 2V \quad V_{BC} = I_1 \cdot 5 = \frac{1}{2}V \quad V_{AD} = V_{AB} + V_{BD} = 10 + 2 = 12V$$

b) They are three resistors in parallel between B and D: $\frac{1}{R_{BD}} = \frac{1}{20} + \frac{1}{40} + \frac{1}{20} = \frac{5}{40} \Rightarrow R_{BD} = \frac{40}{5} = 8\Omega$

$$R_{AD} = R_{AB} + R_{BD} = 40 + 8 = 48\Omega$$

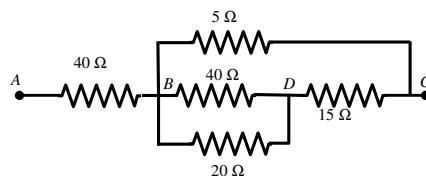c) Between points A and C, the before circuit can be drawn is this way:



Between B and D, resistors of 40 and 20 Ω are connected in parallel: $\frac{1}{R'_{BD}} = \frac{1}{20} + \frac{1}{40} = \frac{3}{40} \Rightarrow R'_{BD} = \frac{40}{3}\Omega$

$$R'_{BC} = \frac{40}{3} + 15 = \frac{85}{3}\Omega \quad \frac{1}{R_{BC}} = \frac{1}{\frac{85}{3}} + \frac{1}{5} = \frac{3}{85} + \frac{1}{5} = \frac{20}{85} = \frac{4}{17} \Rightarrow R_{BC} = \frac{17}{4}\Omega \quad R_{AC} = 40 + \frac{17}{4} = \frac{177}{4}\Omega$$

Form

Electrostatics

$$\vec{F} = K \frac{q_1 q_2}{r^2} \vec{u}_r \quad \vec{E} = \frac{\vec{F}}{q} \quad K = \frac{1}{4\pi\epsilon_0} = 9 \cdot 10^9 \text{ (S.I.)} \quad V_A - V_B = \int_A^B \vec{E} \cdot d\vec{r}$$

$$\vec{E} = K \frac{q}{r^2} \vec{u}_r \quad V = K \frac{q}{r} \quad \int_S \vec{E} \cdot d\vec{S} = \frac{\sum Q}{\epsilon_0} \quad W_{AB} = q(V_A - V_B)$$

Conductors and capacitors

$$E = \frac{\sigma}{\epsilon_0} \quad C = \frac{Q}{V} \quad C = \frac{\epsilon_0 S}{d}$$

$$C_{eq} = \sum C_i \quad \frac{1}{C_{eq}} = \sum \frac{1}{C_i} \quad E_d = \frac{E}{\epsilon_r} \quad C_d = \epsilon_r C \quad W = \frac{Q^2}{2C} = \frac{QV}{2} = \frac{V^2 C}{2}$$

Direct Current

$$\vec{J} = n \cdot e \cdot \vec{v}_a \quad \vec{J} = \sigma \cdot \vec{E} \quad R = \frac{V_1 - V_2}{I} \quad R = \rho \frac{L}{S}$$

$$\rho = \rho_0 (1 + \alpha(T - T_0)) \quad P_R = IV = I^2 R = \frac{V^2}{R}$$