




1. (2,5 points) When the battery of a car becomes empty, it must be recharged by connecting the battery to a power supply. Therefore, **the battery is acting as a receptor**. The intensity needed to charge the battery is  $I=4\text{ A}$  constant during the charging process. The contraelectromotive force of the battery is  $\varepsilon'=12\text{ V}$  and its internal resistance  $r'=0,5\ \Omega$ . The resistance of the wires can be represented through a resistor of  $0,5\ \Omega$ , and the internal resistance of the power supply can be neglected as can be seen in the picture. Find:

- (0,7) The **electromotive force** of the power supply.
- (0,6) The **difference of potential** between points **A and B**.
- (0,6) The **powers** put into play on power supply, battery and resistor ( $P_g$ ,  $P_t$ ,  $P_{r'}$ ,  $P_c$  and  $P_R$ ). State a **balance of power**.
- (0,3) Compute the **efficiency of battery**.
- (0,3) If the charging process takes **10 h**, compute the total energy stored in the battery. The main parameter of a battery is usually given in **A·h**. Which quantity can be measured in **A·h**?

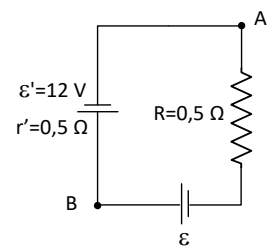1. (2,5 puntos) Cuando la batería de un coche se descarga, debe recargarse conectándola a una fuente de alimentación. Entonces, **la batería actúa como un receptor**. La corriente necesaria para recargar la batería es de  $I=4\text{ A}$  constante durante toda la carga. La fuerza contraelectromotriz de la batería es  $\varepsilon'=12\text{ V}$  y su resistencia interna  $r'=0,5\ \Omega$ . La resistencia de los cables puede representarse mediante una resistencia de  $0,5\ \Omega$ , y la resistencia interna de la fuente de alimentación puede despreciarse, como puede verse en el dibujo. Calcula:

- (0,7) La **fuerza electromotriz** de la fuente de alimentación.
- (0,6) La **diferencia de potencial** entre los puntos **A y B** del circuito.
- (0,6) Las **potencias** puestas en juego en la fuente de alimentación, batería y resistencia ( $P_g$ ,  $P_t$ ,  $P_{r'}$ ,  $P_c$  and  $P_R$ ). Haz un **balance de potencias**.
- (0,3) Calcula el **rendimiento** de la **batería**.
- (0,3) Si el proceso de carga dura **10 h**, calcula la energía total almacenada en la batería. El principal parámetro de una batería se da, normalmente, en **A·h**. ¿Qué magnitud se mide en **A·h**?



**Solution:**

- a) In order the battery acts as a receptor, the intensity must flow in clockwise direction. Then:

$$I = \frac{\sum(\varepsilon + \varepsilon')}{\sum R} = 4 = \frac{\varepsilon - 12}{1} \Rightarrow \varepsilon = 4 + 12 = 16\text{ V}$$

- b) If we go from A to B along the path with the resistor and the battery:  $V_{AB} = I \sum R - (\varepsilon + \varepsilon') = 4(0,5) - 16 = -14\text{ V}$

c)  $P_g = \varepsilon I = 16 \cdot 4 = 64\text{ w}$        $P_t = \varepsilon' I = 12 \cdot 4 = 48\text{ w}$        $P_{r'} = I^2 r' = 16 \cdot 0,5 = 8\text{ w}$        $P_c = P_t + P_{r'} = 48 + 8 = 56\text{ w}$

$P_R = I^2 R = 16 \cdot 0,5 = 8\text{ w}$  Obviously, the generated power must be equal to the consumed power:

$$P_g = P_c + P_R \Rightarrow 64 = 56 + 8$$

d)  $\eta' = \frac{P_t}{P_c} = \frac{48}{56} \approx 0,86 \Rightarrow \eta'$  is near 86%

e)  $10\text{ h} = 3600 \cdot 10 = 36000\text{ s}$ . Therefore  $W = P_t \cdot t = 48 \cdot 36000 = 1728\text{ kJ}$


A is a unit of intensity of current (charge/time). The product of an intensity by a time is a charge. Therefore, the A·h is a unit of electric charge.

2. (3 points) Given the circuit on picture, compute:

- (1) Intensity of current flowing along each branch with the shown directions,  $I_1$ ,  $I_2$  and  $I_3$ . Say if devices  $\varepsilon_1$  and  $\varepsilon_2$  are acting as generators or receptors.
- Potential of point B.
- (1) Thevenin's equivalent generator between points B and D, clearly showing its polarity.
- (0,5) A new branch (that shown on right) is connected between points B and D. Is the 6 V generator of the new branch, generating or consuming energy? Compute its generated or consumed power.
- (0,5) Thevenin's equivalent generator between points A and C, clearly showing its polarity.

2. (3 puntos) Dado el circuito de la figura, calcula:

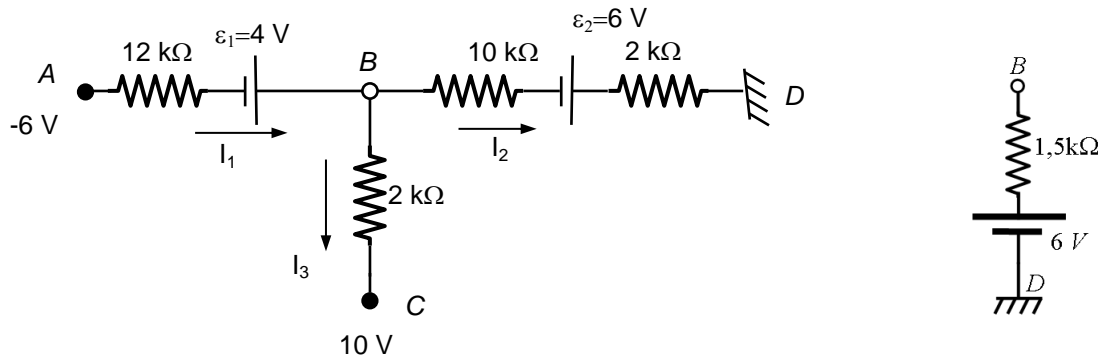- (1) La intensidad de corriente en cada rama con los sentidos mostrados,  $I_1$ ,  $I_2$  y  $I_3$ . Indica si los elementos  $\varepsilon_1$  y  $\varepsilon_2$  actúan como generadores o receptores.
- Potencial del punto B.
- (1) El generador equivalente de Thevenin entre los puntos B y D, indicando claramente su polaridad.
- (0,5) Al circuito se le añade una nueva rama (la mostrada a la derecha) entre los puntos B y D. Indica si el elemento de 6 V de la nueva rama, genera o consume energía y calcula su valor.
- (0,5) El generador equivalente de Thevenin entre los puntos A y C, indicando claramente su polaridad.



**Solution:**


This is a network with 2 junctions and two loops, and so we'll need one equation for junctions and two equations for loops:

$$a) \left. \begin{aligned} I_1 &= I_2 + I_3 \\ V_{AD} &= -6 = 12I_1 - 4 + 12I_2 - 6 \\ V_{CD} &= 10 = -2I_3 + 12I_2 - 6 \end{aligned} \right\} \Rightarrow I_1 = -\frac{17}{24} \text{ mA} \quad I_2 = \frac{25}{24} \text{ mA} \quad I_3 = -\frac{7}{4} \text{ mA}$$

According the computed intensities,  $\varepsilon_1$  is acting as a receptor and  $\varepsilon_2$  is acting as a generator.

$$b) V_{BC} = V_B - 10 = 2I_3 = 2 \cdot \left(-\frac{7}{4}\right) = -\frac{7}{2} \Rightarrow V_B = 10 - \frac{7}{2} = \frac{13}{2} \text{ V}$$

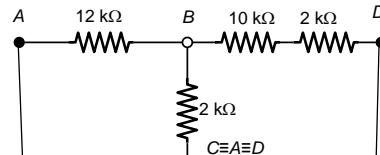
$$c) \varepsilon_T = V_{BD} = V_B - V_D = \frac{13}{2} - 0 = \frac{13}{2} \text{ V}$$



Passive circuit after removing all the generators is

and its equivalent resistance between B and D:

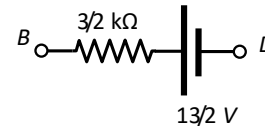
$$\frac{1}{R_{eqBD}} = \frac{1}{10} + \frac{1}{2} + \frac{1}{10+2} \Rightarrow R_{eqBD} = \frac{3}{2} \text{ k}\Omega$$



So, Thevenin's equivalent generator between B and C is:

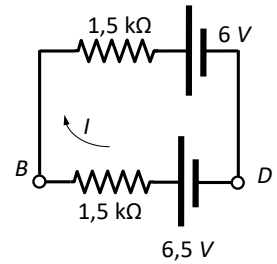- d) If we connect the new branch between points B and D, the resulting circuit is that on picture. The intensity flowing in clockwise direction is:

$$I = \frac{6,5 - 6}{3} = \frac{1}{6} \text{ mA}$$




The 6 V battery of the new branch is consuming energy. The consumed power is

$$P_c = \varepsilon' I = 6 \cdot \frac{1}{6} = 1 \text{ mW}$$

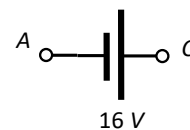- d)  $\varepsilon_T = V_{AC} = -6 + 10 = -16 \text{ V}$  And  $R_{eqAC} = 0$

Therefore, the Thevenin's equivalent generator between A and C is




**3. (2 points)** The rectangular solenoid on picture, with cross section  $6 \times 4 = 24 \text{ cm}^2$  is flowed by a current  $I = 4 \text{ A}$  in the shown direction. It makes a  $60^\circ$  angle with the positive direction of the Y axis, and tge number of turns is 500. Compute:

- (0,8) The magnetic moment  $\vec{\mu}$  of the solenoid.
- (0,6) The torque  $\vec{\tau}$  of the forces acting on it when a uniform magnetic field  $\vec{B} = 2\vec{i} - 3\vec{j} \text{ T}$  is applied.
- (0,6) The force acting on the side of solenoid lying on the Z axis.

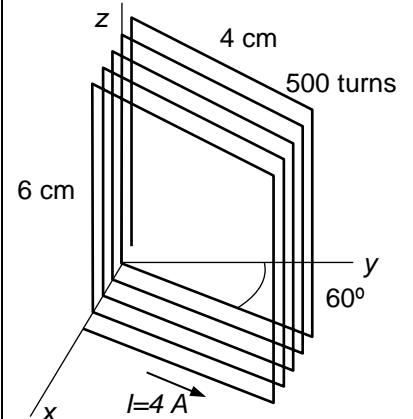**3. (2 puntos)** La bobina rectangular de la figura, de sección  $6 \times 4 = 24 \text{ cm}^2$  está recorrida por una corriente  $I = 4 \text{ A}$  en el sentido indicado. Forma un ángulo de  $60^\circ$  con la dirección positiva del eje Y, y tiene 500 espiras. Calcula:

- (0,8) El momento magnético de la bobina,  $\vec{m}$ .
- (0,6) El momento  $\vec{M}$  de las fuerzas que actúan sobre ella si se le aplica un campo magnético uniforme  $\vec{B} = 2\vec{i} - 3\vec{j} \text{ T}$ .
- (0,6) La fuerza que actúa sobre el lado de la bobina coincidente con el eje Z.



**Solution:**


a)  $\vec{\mu} = NI\vec{S} = 500 \cdot 4 \cdot 24 \cdot 10^{-4} (\cos 60^\circ \vec{i} - \sin 60^\circ \vec{j}) = 2,4\vec{i} - 4,2\vec{j} \text{ Am}^2$

b)  $\vec{\tau} = \vec{\mu} \times \vec{B} = (2,4\vec{i} - 4,2\vec{j}) \times (2\vec{i} - 3\vec{j}) = \begin{vmatrix} \vec{i} & \vec{j} & \vec{k} \\ 2,4 & -4,2 & 0 \\ 2 & -3 & 0 \end{vmatrix} = (-7, 2 + 8, 4)\vec{k} = 1,2\vec{k} \text{ Nm}$

c)  $\vec{F}_1 = NI\vec{L} \times \vec{B} = 500 \cdot 4 \cdot (-6 \cdot 10^{-2} \vec{k}) \times (2\vec{i} - 3\vec{j}) = -360\vec{i} - 240\vec{j} \text{ N}$

**4. (2,5 points)** Two **infinite** straight carrying current **conductors** are placed on **plane YZ**, lying on **axes Y and Z** respectively. They carry equal currents  $I=I_1=I_2$ , being the direction of  $I_2$  that shown on picture. The **modulus** of magnetic field at point **A(0,2,2) m** is  $B_A=10^{-5} \text{ T}$ . Find:  
 a) (0,6) The **direction of current  $I_1$**  (to up or to down) and the **direction of magnetic field** at point **A** ( $+\vec{i}$  or  $-\vec{i}$ ). **Justify** the answer.  
 b) (0,6) The **magnitude of I**.  
 c) (0,7) The **magnetic field vector** at point **B(0,2,1) m**.  
 d) (0,6) Give the **coordinates** of a point where the **magnetic field was null**.

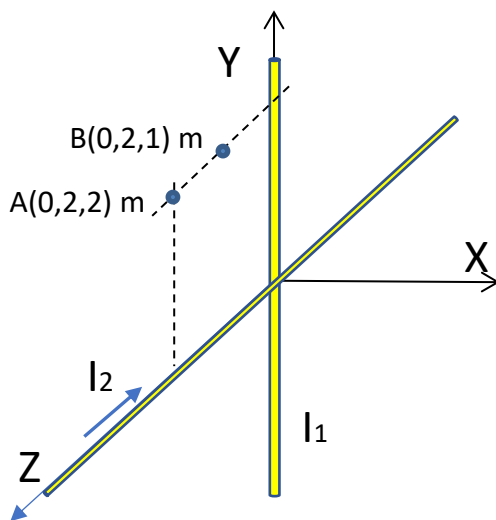**4. (2,5 puntos)** Dos **conductores** rectilíneos e **indefinidos** están colocados en el **plano YZ**, sobre los **ejes Y y Z**, respectivamente. Llevan corrientes iguales  $I=I_1=I_2$ , siendo la dirección de  $I_2$ , la mostrada en la figura. El **módulo** del campo magnético en el punto **A(0,2,2) m** es  $B_A=10^{-5} \text{ T}$ . Halla:  
 a) (0,6) La **dirección de la corriente  $I_1$**  (hacia arriba o hacia abajo), y la **dirección del campo magnético** en **A** ( $+\vec{i}$  ó  $-\vec{i}$ ). **Justifica** la respuesta.  
 b) (0,6) El **valor de I**.  
 c) (0,7) El **vector campo magnético** en el punto **B(0,2,1) m**.  
 d) (0,6) Da las **coordenadas** de un punto donde se **anule el campo magnético**.



**Solution:**

On every case, the magnetic field is the summatory of magnetic field produced by each conductor:

a) If  $I_1$  was flowing to downwards, then the magnetic field at point A would be null. Therefore,  $I_1$  has to flow upwards. Then, the magnetic field at point A must go in the positive direction of X axis,  $+\vec{i}$ .

b)  $\vec{B}_A = \vec{B}_1 + \vec{B}_2 = \frac{\mu_0 I}{2\pi \cdot 2} \vec{i} + \frac{\mu_0 I}{2\pi \cdot 2} \vec{i} = \frac{\mu_0 I}{2\pi} \vec{i} = 2I \cdot 10^{-7} \vec{i}$

According the statement  $2I \cdot 10^{-7} = 10^{-5} \Rightarrow I = 50 \text{ A}$

c)  $\vec{B}_B = \vec{B}_1 + \vec{B}_2 = \frac{\mu_0 I}{2\pi \cdot 1} \vec{i} + \frac{\mu_0 I}{2\pi \cdot 2} \vec{i} = \frac{3\mu_0 I}{4\pi} \vec{i} = 3I \cdot 10^{-7} \vec{i} = 150 \cdot 10^{-7} \vec{i} = 15 \cdot 10^{-6} \vec{i} \text{ T}$

d) The magnetic field can only be null at points over the plane YZ, on second and fourth quadrants. Moreover, as the intensities on both conductors are equal, these points must be placed over the angle bisector of such quadrants. For example, the point (0,-1,1) would be a point where the magnetic field would be null.

## FORM

**Direct current**  $V_A - V_B = I \sum R - \sum \mathcal{E}$   $I = \frac{\sum \mathcal{E}}{\sum R}$   $P = V \cdot I$   $\mathcal{E} = \frac{dW}{dq}$   $P_R = I^2 \cdot R$   $P_g = \mathcal{E} \cdot I$   $P_t = \mathcal{E}' \cdot I$   $P_g - P_r = P_s$   $P_t + P_r = P_c$

$$\eta_g = \frac{P_s}{P_g} \quad \eta_r = \frac{P_t}{P_c}$$

**Magnetic Forces**  $\vec{F} = q(\vec{v} \times \vec{B})$   $d\vec{F} = I d\vec{l} \times \vec{B}$   $\vec{\mu} = N \cdot I \cdot \vec{S}$   $\vec{\tau} = \vec{\mu} \times \vec{B}$   $V_H = \frac{I \cdot B \cdot d}{n \cdot e \cdot S}$

**Sources of magnetic field**  $d\vec{B} = \frac{\mu_0 I}{4\pi} \frac{d\vec{l} \times \vec{r}}{r^3}$   $\mu_0 = 4\pi 10^{-7} \text{ (I.S. units)}$   $B = \frac{\mu_0 I}{2\pi x}$

$$B = \frac{\mu_0 I}{2R} \oint_L \vec{B} \cdot d\vec{l} = \mu_0 \sum I \quad B = \frac{\mu_0 NI}{l}$$